Presenter Name:				Location: 260
Subject (Circle All That Apply): Science	Technology Enginee	<mark>ring</mark> Arts	Mathematics	
Grade Level (Circle All That Apply):	Middle School	High School	Collegiate	
Topic Title: <u>Short Circuit VR</u>				
	Lesson Foo	cus and Go	oals	
<ul><li>SUBJECT OBJECTIVE:</li><li>1. Be able to problem solve through puzzles involving circuits and also be able to understand what each component of a circuit does.</li></ul>		<ol> <li>JHSL OBJECTIVE:</li> <li>1. Work with students to get them a hands on experience with Virtual Reality technology in the classroom.</li> <li>2. Expose students to critical thinking skills in the STEM field.</li> </ol>		
	Texas Essential Know	ledge and	Skills (TEKS)	
Principles of Technology; c.6.A & c.6.B. & c.6.B. Engineering Design and Present Problem Solving; c.5.A, c.5.B, c.5.C, c.5.I Extended Practicum in Science, Technol	<b>ation I</b> ; c.7.A, c.7.B, c.7.C, c.8.A & D, c.5.F, c.5.G & c.5.K. <b>Practicum i</b>	c.8.B. Engine n Science, Tec	ering Design and Presentat hnology, Engineering, and	tion II; c.8.B. Engineering Design and
Even tl Workfo probler general	<b>Irton Introduction Talk</b> ( <i>approx. 5</i> nough Halliburton is an oil and gas in prce. The Javelina Halliburton STEM n solving skills associated with scier	ndustry, Hallibu I Labs provide aces, technolog nool and underg	if not have been completed burton is also very invested in the opportunities to enhance y, engineering, math and geo graduate students. Halliburto	the next generation of STEM high level critical thinking and
Studen	t Introduction ( <i>approx. 5 minutes</i> ) ts will be introduced to circuits and t , current, and resistance will be expl	*	-	*
3. Level 1	(approx. 5 minutes)			

	ple circuit where we establish a flow of current. Students will use a breadboard, and a gerous overflow of current and voltage.
	rcuit and principles from level one, but this time will be asked to insert an LED. ot enough resistance to stop the circuit from having too much voltage and current.
	evel is identical to level two's, this time you are integrating the switch component to the aced to what the switch is and how to integrate it as well.
Le	arning Objective
	Content Review
<ul> <li>Circuits require a source of power.</li> <li>Electricity is dangerous.</li> </ul>	Students have been asked 1. What is Ohm's Law?
<ul> <li>Circuits can sometimes be complex and require critical thinking to understand.</li> </ul>	2. How much resistance is needed for a circuit with so many volts and amperes?
	3. How do you connect a breadboard to a battery?
	New Content
'tudents will know	Students will be able to
<ul><li>How and when to use Ohm's law when creating a circuit.</li><li>How to follow a diagram when creating a circuit.</li></ul>	<ul> <li>Explain what current, voltage, and resistance is.</li> <li>Understand what a breadboard is and how to form basic connections.</li> <li>Be able to use Ohm's law.</li> </ul>
	Assessment
	Assessment

## **Sources of Information:**

1.